
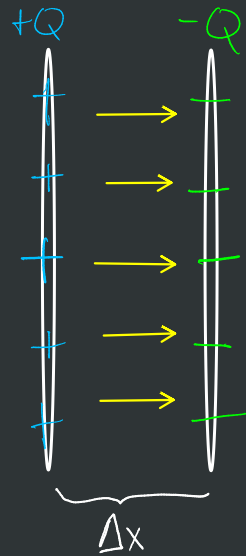


After this you can

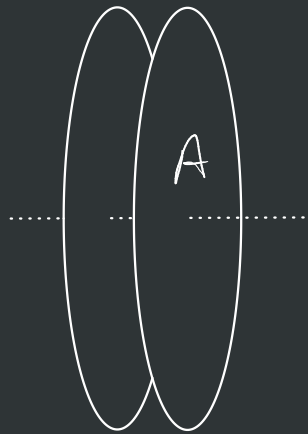- use the new quantity of capacitance to relate the charge stored on a capacitor to the voltage between the plates
- use the physical properties of a capacitor to predict how much charge can be stored
- discuss energy storage in a capacitor



$$\Delta V = E \cdot \Delta x$$


$$\Delta x \cdot E = \frac{Q}{\epsilon_0 A} \cdot \Delta x$$

$$\Delta V = \frac{Q}{\epsilon_0 A} \cdot \Delta x$$

$$\frac{\epsilon_0 A}{\Delta x} = \frac{Q}{\Delta V} = C$$

parallel plate capacitor

$$C = \frac{\epsilon_0 A}{\Delta x}$$

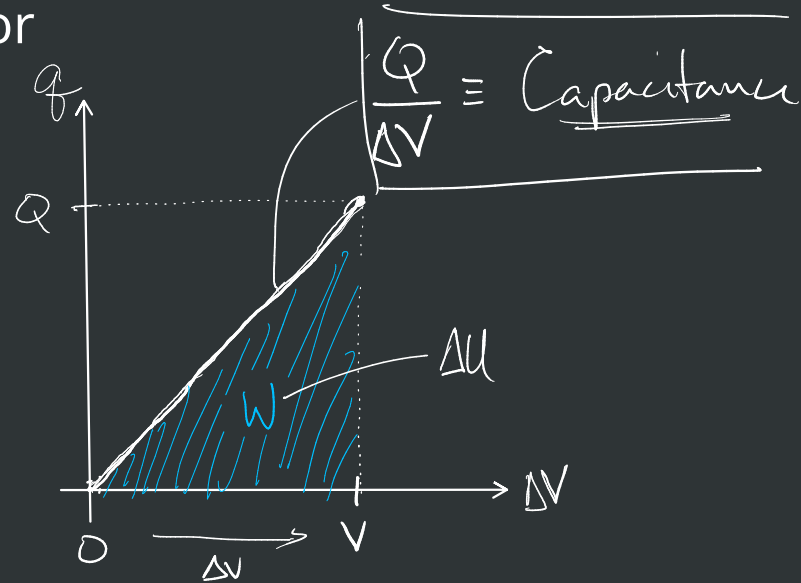

$$\Delta U = \frac{1}{2} \Delta V Q$$

$$C = \frac{Q}{\Delta V}$$

energy stored in a capacitor

Units

$$= \frac{[\text{Coulomb}]}{[\text{Volt}]}$$

$$= \frac{[C \cdot C]}{[J]}$$

$$= [\text{Farad}]$$


$$\mu F \rightarrow 10^{-6} F$$

$$nF \rightarrow 10^{-9} F$$

$$pF \rightarrow 10^{-12} F$$

After this you can

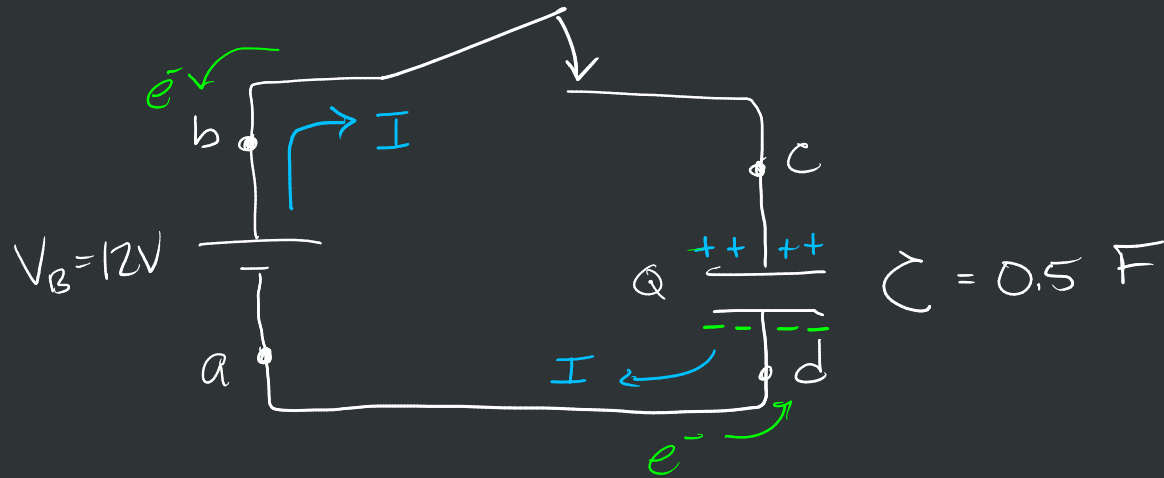- determine the charge stored on a capacitor due to a potential
- determine the equivalent capacitance due to multiple capacitors connected together



$\Delta V_B = \Delta V_C$ ~ then I stops and Q is complete


$$\Delta V_B - \Delta V_C = 0$$

$$\Delta V_B = \Delta V_C$$

$$\frac{Q}{\Delta V_C} = C$$

$$\Delta V_C = \frac{Q}{C}$$

$$\Delta V_B = \frac{Q}{C}$$

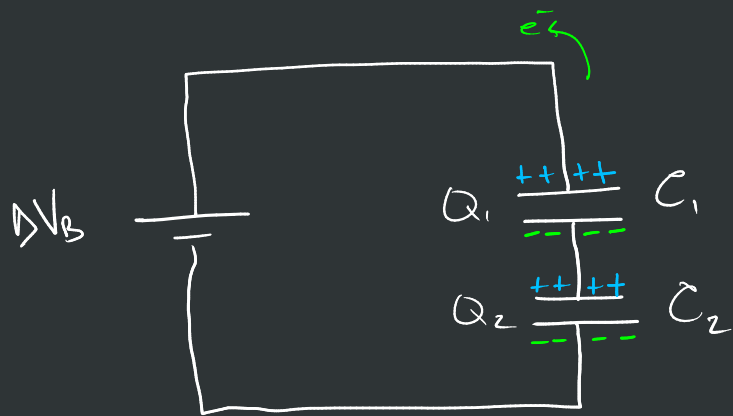

$$Q_1 = Q_2 = Q$$

$$\Delta V_B - \Delta V_1 - \Delta V_2 = 0$$

$$\Delta V_B = \Delta V_1 + \Delta V_2$$


$$\Delta V_B = \frac{Q_1}{C_1} + \frac{Q_2}{C_2}$$

$$\Delta V_B = \frac{Q}{C_1} + \frac{Q}{C_2}$$

$$\Delta V_B = Q \left(\frac{1}{C_1} + \frac{1}{C_2} \right)$$

$$\boxed{\Delta V_B = \frac{Q}{C_E}} \quad \left| \quad C_E = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2} + \dots} \right.$$

Capacitors in series

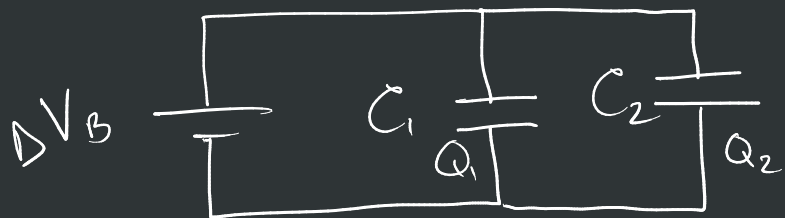

$$\Delta V_B - \Delta V_1 = 0$$

$$\Delta V_B = \frac{Q_1}{C_1}$$

$$Q_1 = \Delta V_B \cdot C_1$$

$$\Delta V_B - \Delta V_2 = 0$$

$$\Delta V_B = \frac{Q_2}{C_2}$$

$$Q_{\text{total}} = Q_1 + Q_2 + \dots$$

$$\Delta V_B = \frac{Q_{\text{total}}}{C_E}$$

$$Q_{\text{total}} = \Delta V_B \cdot C_1 + \Delta V_B \cdot C_2 + \dots$$

$$Q_{\text{total}} = \Delta V_B (C_1 + C_2 + \dots)$$


$$\Delta V_B = \frac{Q_{\text{total}}}{C_1 + C_2 + \dots}$$

$$C_E = C_1 + C_2 + \dots$$

capacitors in parallel

After this you can

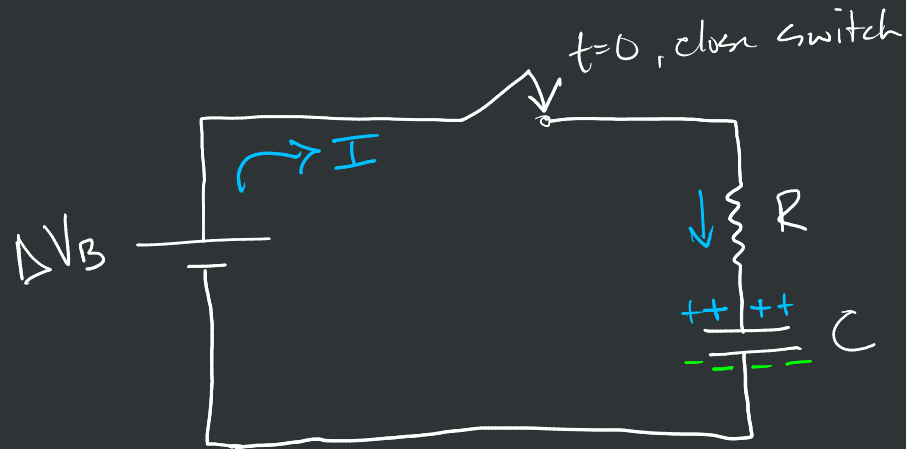- describe the exponential behavior of RC circuits
- use the relationships for current or charge to solve for an unknown quantity



$$\Delta V_B - \Delta V_R - \Delta V_C = 0$$

$$\Delta V_B = \Delta V_R + \Delta V_C$$

$$I(t) \cdot R \quad \Delta V_C = \frac{Q(t)}{C}$$

$t=0$



$$\Delta V_C = 0$$

$$\Delta V_R = \Delta V_B = I_0 \cdot R$$

$t = \text{long time}$

$$\Delta V_C = \Delta V_B \Rightarrow Q_{\max} = V_B \cdot C$$

$$\Delta V_R = 0$$

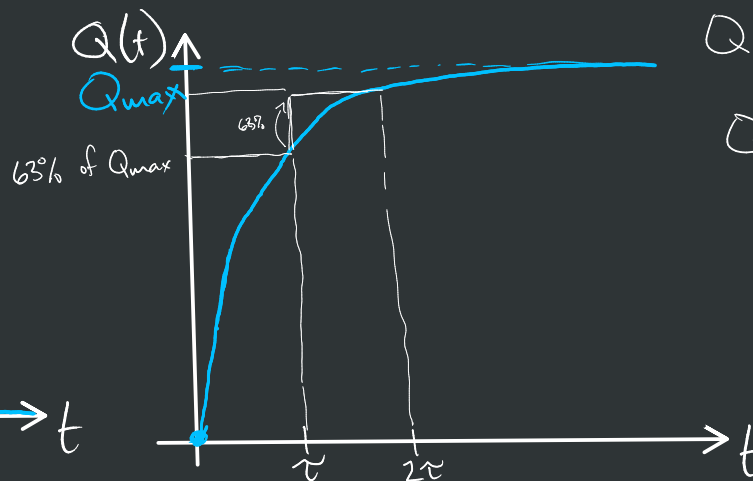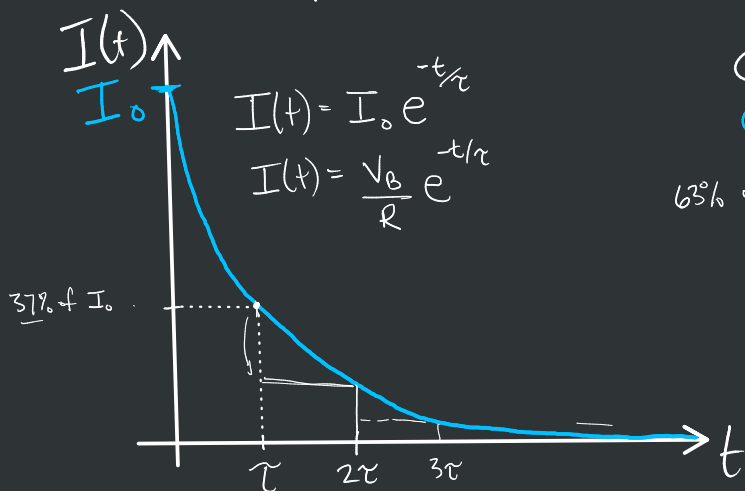


$$Q(t) = Q_{\max} (1 - e^{-t/\tau})$$

$$Q(t) = V_B \cdot C (1 - e^{-t/\tau})$$

$\tau = R \cdot C$
seconds


charging a capacitor

discharging a capacitor

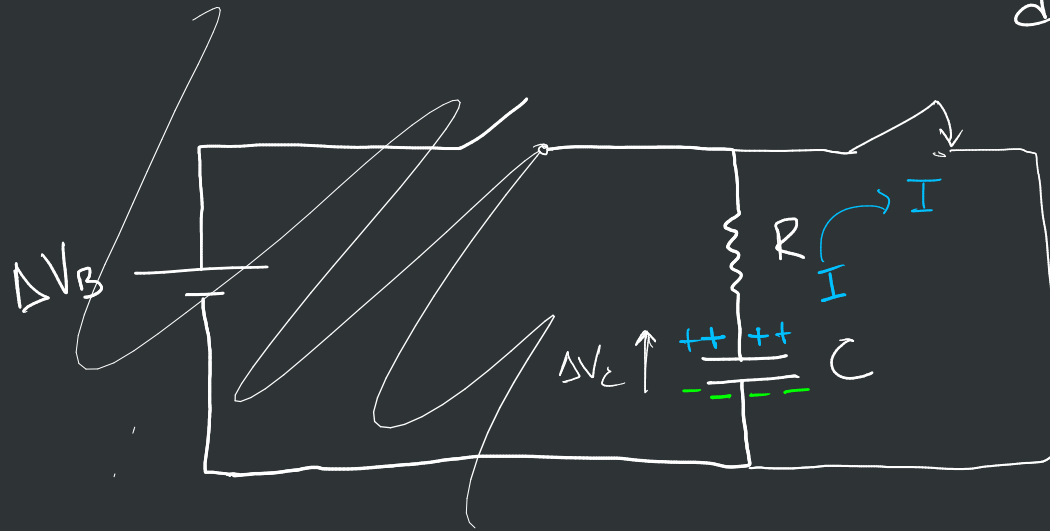


$$\Delta V_C - \Delta V_R = 0$$

$$\Delta V_C = \Delta V_R$$

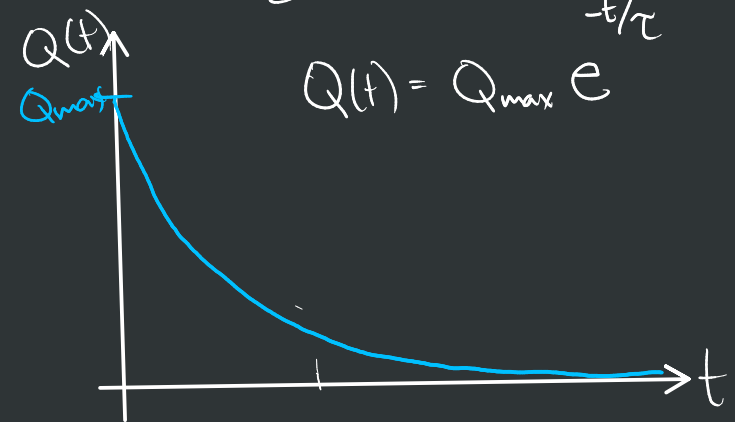

$$Q(t) = Q_{\max} e^{-t/\tau}$$

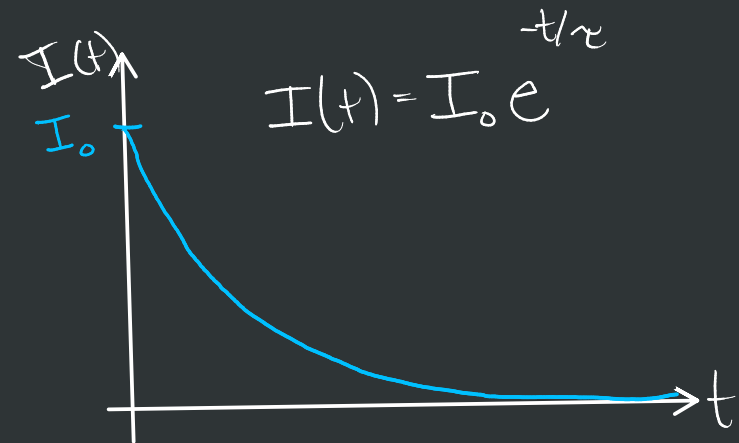

$$I(t) = I_0 e^{-t/\tau}$$

