



Chapter 18 - Circuits - resistance

After this you can

- discuss the new quantity of current → flow of charge
- differentiate the direction of current in real devices

$$I = \frac{\text{number of charges}}{\text{time interval}}$$

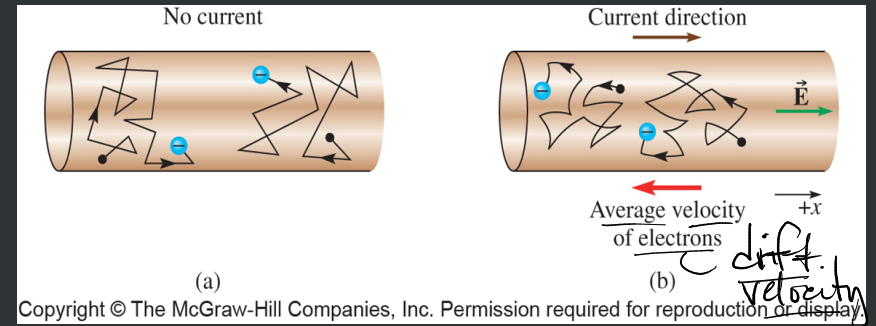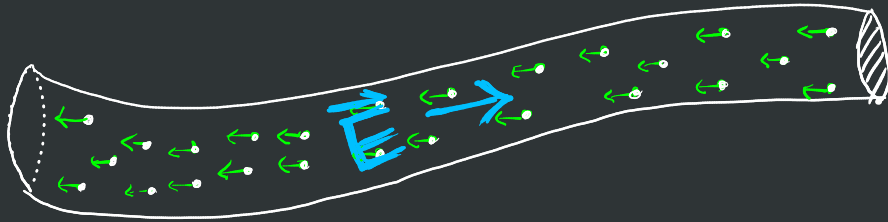
$$\left[\frac{C}{s} \right] = [Ampere] = [Amps] = [A]$$



Conditions for current flow:

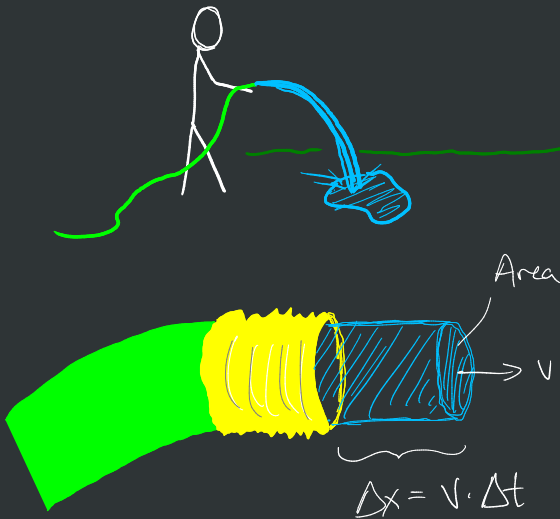1. charges present in a region
2. charge are free to move
3. electric field is present

} metal conducting wire
↳ only electrons move



Volumetric flow rate:

$$\frac{\Delta V}{\Delta t} = A \cdot v$$

mass flow rate:

$$\frac{\Delta m}{\Delta t} = \rho_m \cdot A \cdot v$$

↳ kg/m^3


charge flow rate:

$$I = \frac{\Delta q}{\Delta t} = \rho_c \cdot A \cdot v$$

↳ charge density


$$I = e \cdot n \cdot A \cdot v$$

↳ C/m^3

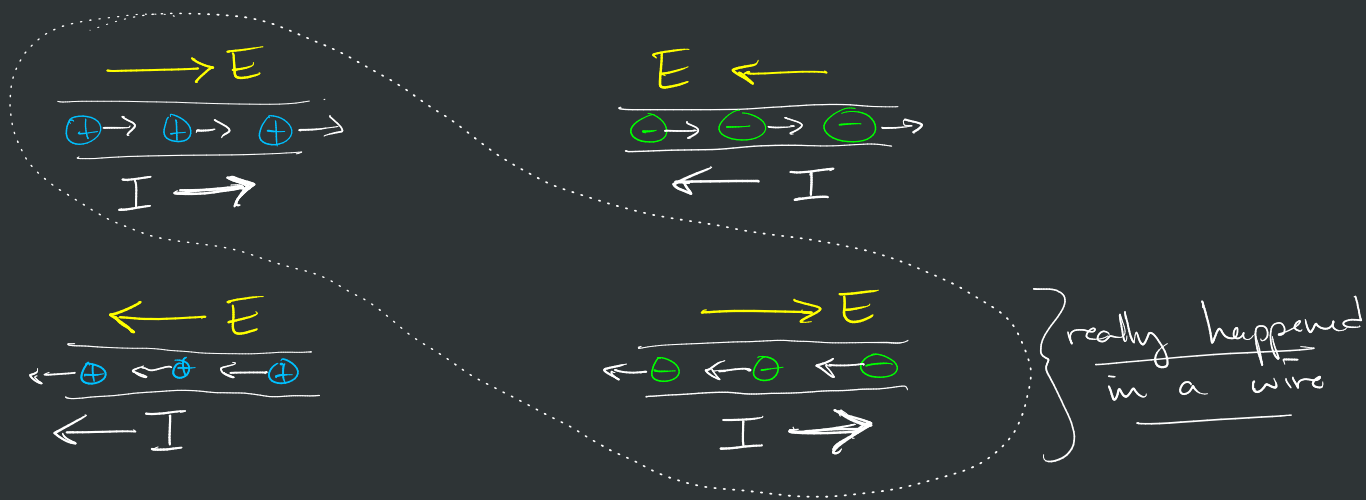


After this you can

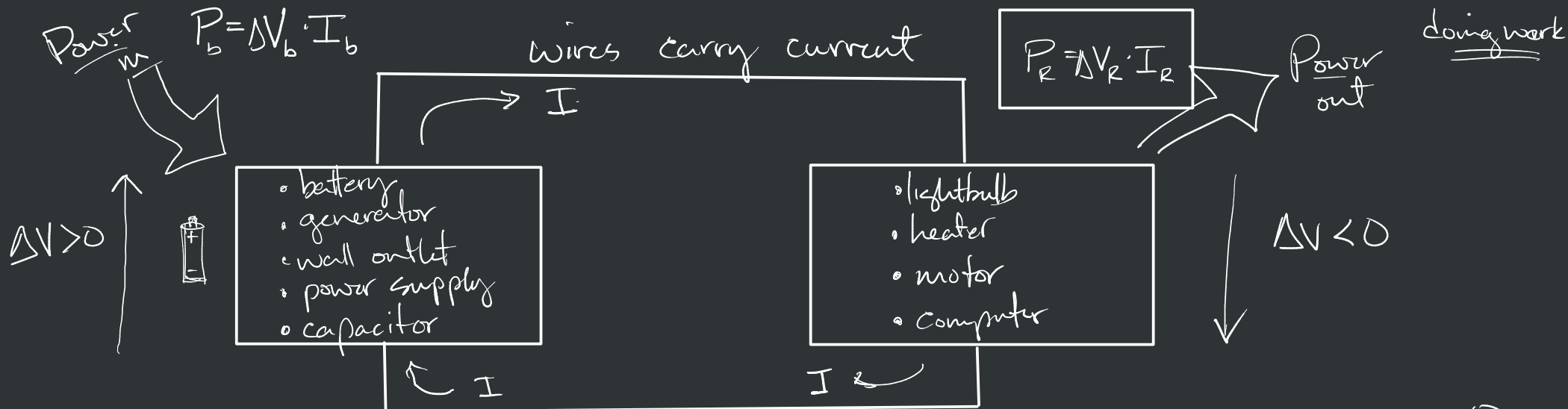- discuss the construction of a circuit
- use Ohm's law to determine the resistance of a circuit
- discuss power input and output in circuits



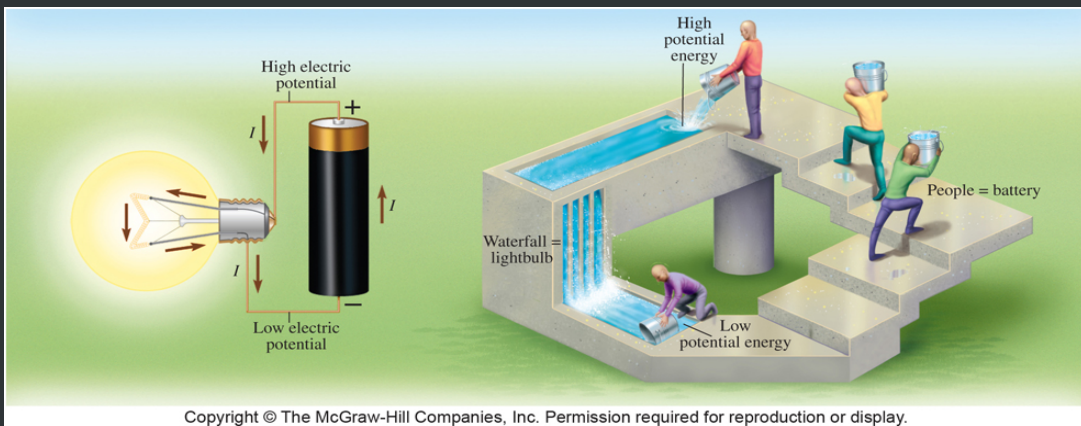Conservation of Energy \rightarrow potential increases + potential decreases = 0



Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

Ohm's Law

$$I \propto \Delta V$$

$$\left[\frac{V}{A} \right] = [\text{Ohms}]$$

$$= [\Omega]$$

$$\frac{\Delta V}{I} = \text{Resistance}$$

$$\Delta V = I \cdot R$$

idealized resistor

$$R = 100 \Omega$$

Resistance in a wire:



$$R = \rho \frac{l}{A}$$

resistivity

Table 18.1 Resistivities and Temperature Coefficients at 20°C


	$\rho (\Omega \cdot m)$	$\alpha (^\circ C^{-1})$		$\rho (\Omega \cdot m)$	$\alpha (^\circ C^{-1})$
Conductors			Semiconductors (pure)		
Silver	1.59×10^{-8}	3.8×10^{-3}	Carbon	3.5×10^{-5}	-0.5×10^{-3}
Copper	1.67×10^{-8}	4.05×10^{-3}	Germanium	0.6	-50×10^{-3}
Gold	2.35×10^{-8}	3.4×10^{-3}	Silicon	2300	-70×10^{-3}
Aluminum	2.65×10^{-8}	3.9×10^{-3}			
Tungsten	5.40×10^{-8}	4.50×10^{-3}			
Iron	9.71×10^{-8}	5.0×10^{-3}	Insulators		
Lead	21×10^{-8}	3.9×10^{-3}	Glass	$10^{10} - 10^{14}$	
Platinum	10.6×10^{-8}	3.64×10^{-3}	Lucite	$> 10^{13}$	
Manganin	44×10^{-8}	0.002×10^{-3}	Quartz (fused)	$> 10^{16}$	
Constantan	49×10^{-8}	0.002×10^{-3}	Rubber (hard)	$10^{13} - 10^{16}$	
Mercury	96×10^{-8}	0.89×10^{-3}	Teflon	$> 10^{13}$	
Nichrome	108×10^{-8}	0.4×10^{-3}	Wood	$10^8 - 10^{11}$	

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.


After this you can

- discuss the difference between resistors connected in series and resistors connected in parallel
- use the conservation of energy to set up an equation to solve for an unknown quantity in a circuit "emf"

Example

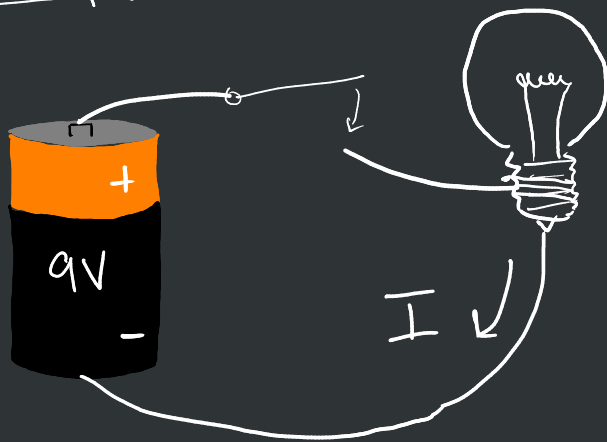

\mathcal{E}
+9V = ΔV_b

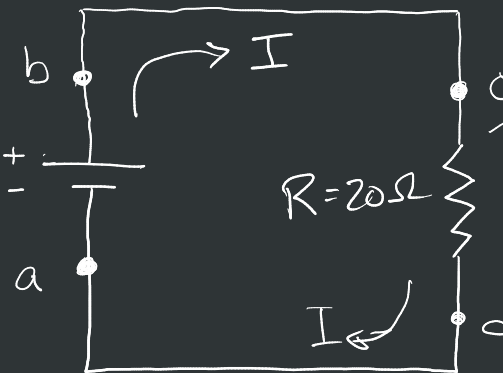

$$P_b = \Delta V_b \cdot I_b$$
$$= 9V \cdot 0.45 A$$
$$P_b = 4.05 \text{ Watts}$$

$$P_R = \Delta V_R \cdot I_R$$
$$= 9V \cdot 0.45 A$$
$$P_R = 4.05 \text{ Watts}$$

→ loop around the circuit

$$+\Delta V_b - \Delta V_R = 0$$

$$\Delta V_b = \Delta V_R$$

Ohm's Law



$$\Delta V_R = I \cdot R$$

$$\Delta V_b = I \cdot R$$

$$\frac{\Delta V_b}{R} = I \quad \rightarrow \quad \frac{9V}{20\Omega} = I = 0.45 A$$

Resistors in series

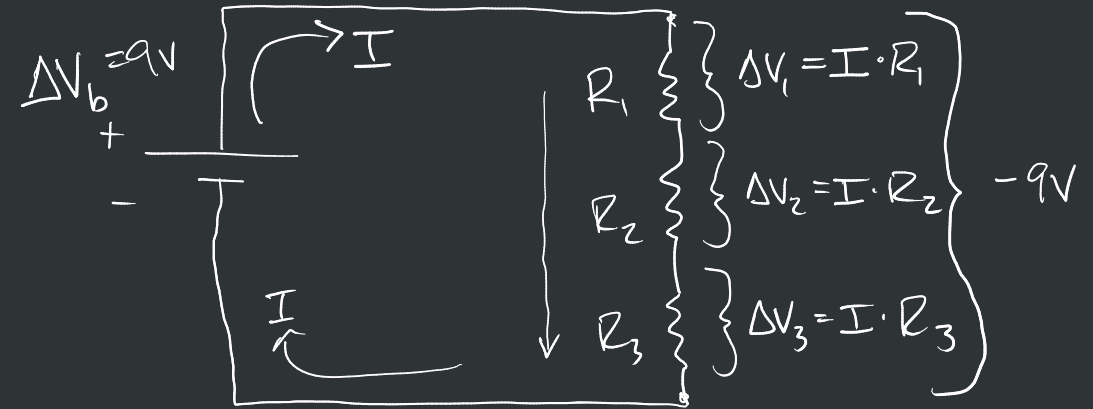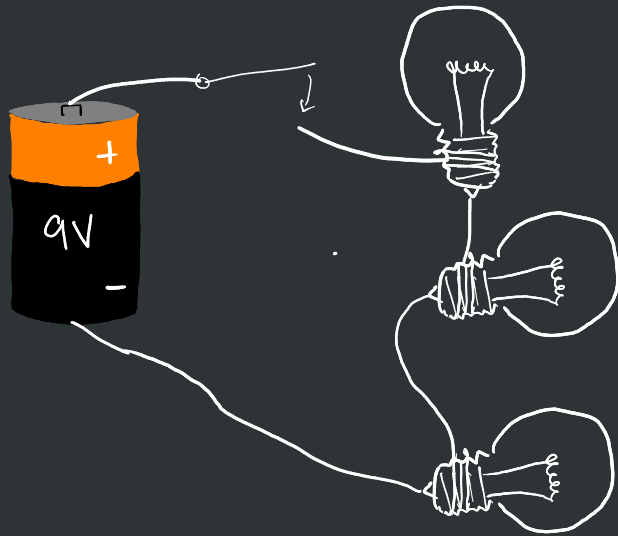- resistors connected end to end
- one pathway out of the battery
- current is the same through each resistor



$$\text{loop} \rightarrow +\Delta V_b - \Delta V_1 - \Delta V_2 - \Delta V_3 = 0$$

$$\Delta V_b = \Delta V_1 + \Delta V_2 + \Delta V_3$$

$$\Delta V_b = IR_1 + IR_2 + IR_3$$



Equivalent Resistance of Resistors in Series

$$\Delta V_b = I(R_1 + R_2 + R_3) \Rightarrow \frac{\Delta V_b}{R_E} = I$$

$$\underline{R_E} = R_1 + R_2 + R_3 + \dots$$

Resistors in parallel

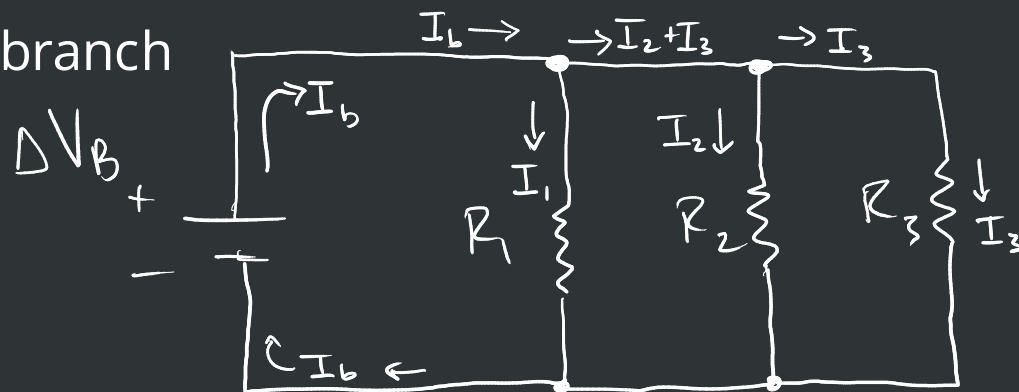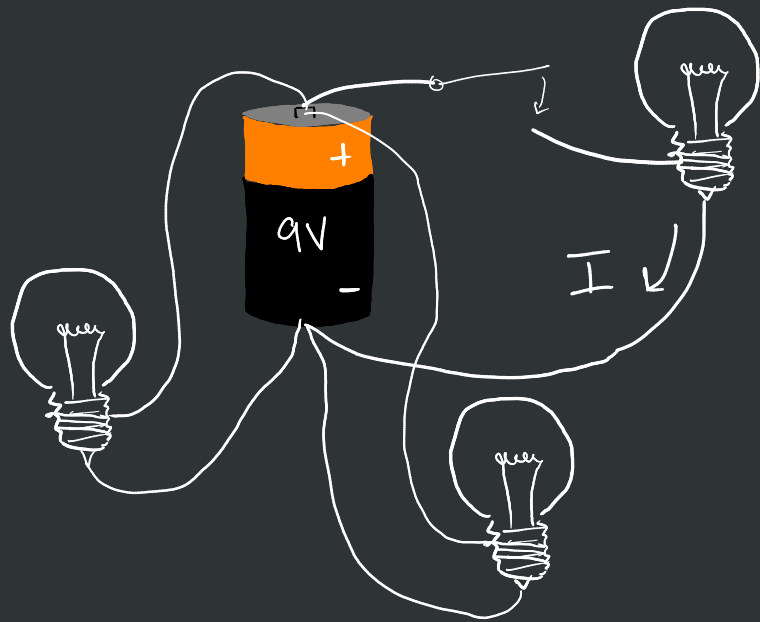- each resistor has its own connection to the power supply
- potential drop is the same across each resistor
- current through the battery is the sum of the currents through each branch



$$\begin{array}{l|l|l} \Delta V_b - \Delta V_1 = 0 & \Delta V_b - \Delta V_2 = 0 & \Delta V_b - \Delta V_3 = 0 \\ \Delta V_b = I_1 R_1 & \Delta V_b = I_2 R_2 & \Delta V_b = I_3 R_3 \\ I_1 = \frac{\Delta V_b}{R_1} & & \end{array}$$

$$I_b = I_1 + I_2 + I_3$$

$$I_b = \frac{\Delta V_b}{R_1} + \frac{\Delta V_b}{R_2} + \frac{\Delta V_b}{R_3}$$

$$\Delta V_b = I_b \cdot R_E$$

$$I_b = \Delta V_b \frac{\left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)}{\left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right) \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)}$$

$$\Delta V_b = I_b \cdot \boxed{\frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}}} \quad R_E$$

$$\rightarrow R_E = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots}$$

$$\frac{1}{R_E} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots$$

from the book

